

# Torrot Muvi Controller Replacement

## Selected Controller:


Kellys – sine wave BLDC controller KLS7215N

 <https://kellycontroller.com/shop/brushless/>

## Torrot Architecture:

- The original Torrot controller, display, and batteries communicate over a CAN-bus — *this is not used in the new setup.*
- The scooter contains two DC-DC step-down converters (72V → 12V):
  - One is powered immediately after the battery is connected.
  - The second one (which powers lights, etc.) is only active after the scooter is started.
- Battery 1 is connected via a thin wire to the controller (pin 34) and to one of the DC-DC converters, along with protection components (like GPS, alarm, etc.) — see *the security wiring diagram*. After startup, contactors are closed (controlled by the controller via pins 12 and 13), and the battery is then connected via a thick cable.
- Startup likely works as follows:  
When you turn the key, power is supplied to the display, which most likely sends a signal to the controller. In response, the controller outputs voltage (pin 35) to power the second DC-DC converter. I wasn't able to locate any other source powering that second DC-DC converter.

security wiring diagram

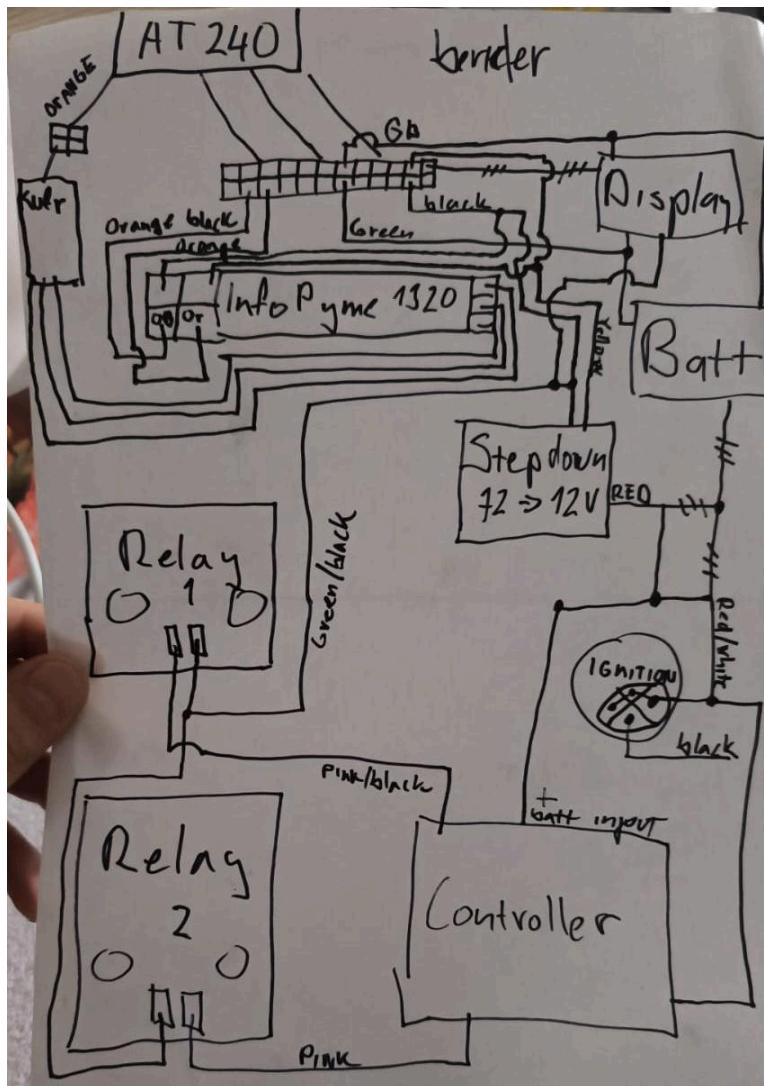

### Torrot pin identification:

(1)	(2)	(3)	(4)	(5)	(6)	(7)	(8)	(9)	(10)	(11)	(12)
(13)	(14)	(15)	(16)	(17)	(18)	(19)	(20)	(21)	(22)	(23)	
(24)	(25)	(26)	(27)	(28)	(29)	(30)	(31)	(32)	(33)	(34)	(35)

(modré)

1. Šípová "černý" displej      11; modrá/signal blinkr      12; oranž. blinkr      12a; oranž. blinkr - pravý  
 2: X      12; růžová + elektrolyt 1. baterie      12b; bílá - černá - bílá      12c; bílá - černá - bílá - pravý  
 3; červ. bílá      13; růžová, černá      13a; bílá - černá - bílá - zleva      13b; bílá - černá - bílá - zprava  
 4; čern. bílá      14; X      14a; bílá - zleva      14b; bílá - zprava  
 5; černá      15; X      15a; bílá - zleva      15b; bílá - zprava  
 6; červ. žlutá - ohlášek Příletka      16; oranž. červ. napajení signálů      16a; bílá - zleva      16b; bílá - zprava  
 7; hřídele      brzdový spináč      17; modrá - červ.      17a; bílá - zleva      17b; bílá - zprava  
 8: X      18; žlutá      18a; bílá - zleva      18b; bílá - zprava  
 9: X      19; zelená      19a; bílá - zleva      19b; bílá - zprava  
 10; žlutá signal blinkr      20; sv. modrá      20a; bílá - zleva      20b; bílá - zprava  
 11; bílá      21; černá - žlutá      21a; bílá - zleva      21b; bílá - zprava  
 12; bílá      22; sv. modrá - černá      22a; bílá - zleva      22b; bílá - zprava  
 13; bílá - černá - bílá - zleva      23; modrá - černá - bílá - zprava      23a; bílá - zleva      23b; bílá - zprava

**Zadní brzdové světlo**

24; bílá - zleva      24a; bílá - zprava  
 25; bílá - zleva      25a; bílá - zprava  
 26; bílá - černá - zleva      26a; bílá - černá - zprava  
 27; bílá - zleva      27a; bílá - zprava  
 28; bílá - zleva      28a; bílá - zprava  
 29; bílá - zleva      29a; bílá - zprava  
 30; bílá - zleva      30a; bílá - zprava  
 31; bílá - zleva      31a; bílá - zprava  
 32; bílá - zleva      32a; bílá - zprava  
 33; bílá - zleva      33a; bílá - zprava  
 34; bílá - zleva      34a; bílá - zprava  
 35; bílá - zleva      35a; bílá - zprava


+ 12V      - 12V

+ 12V      - 12V



DC/DC  
zdroj

Zapal. in

### "Ignition" diagram

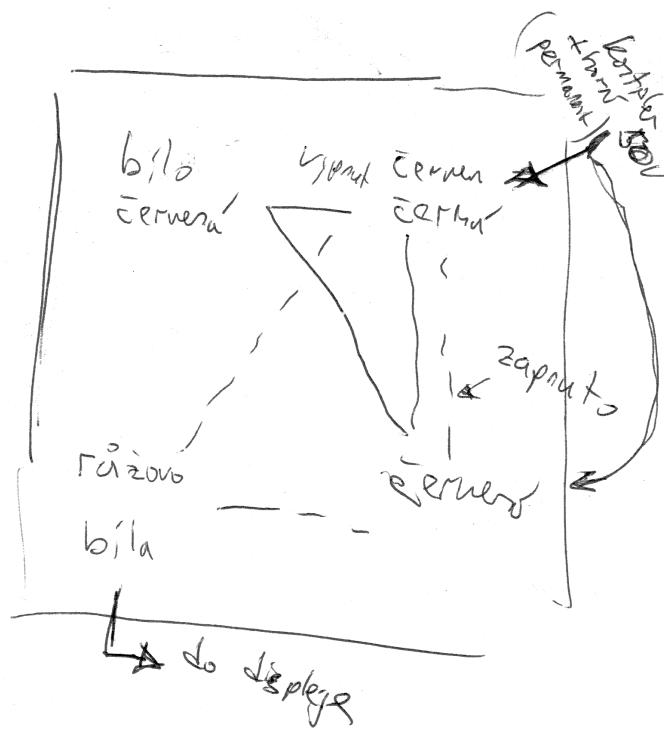


### “9pin diagram (blinkers)”

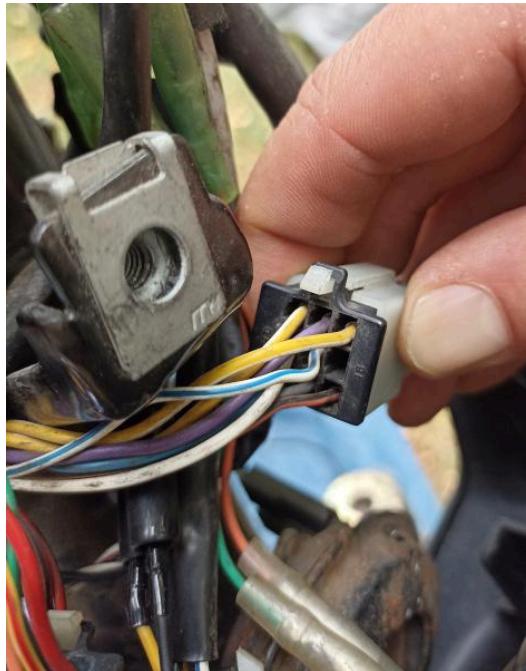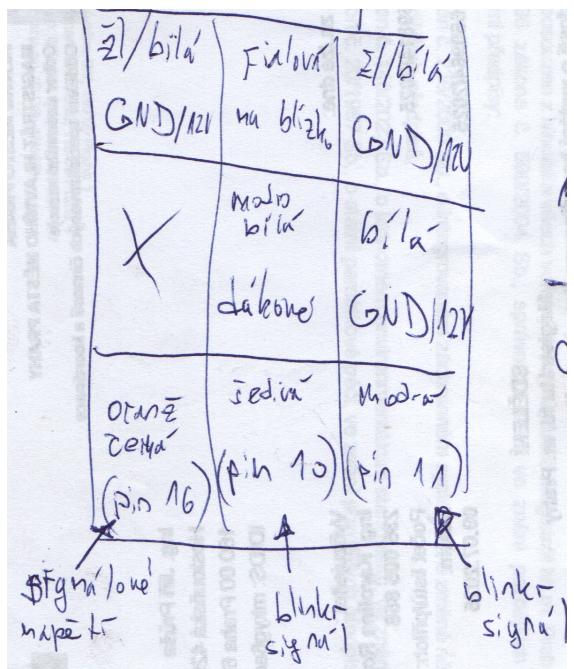


## Kellys - KLS7215N

Connection diagram:

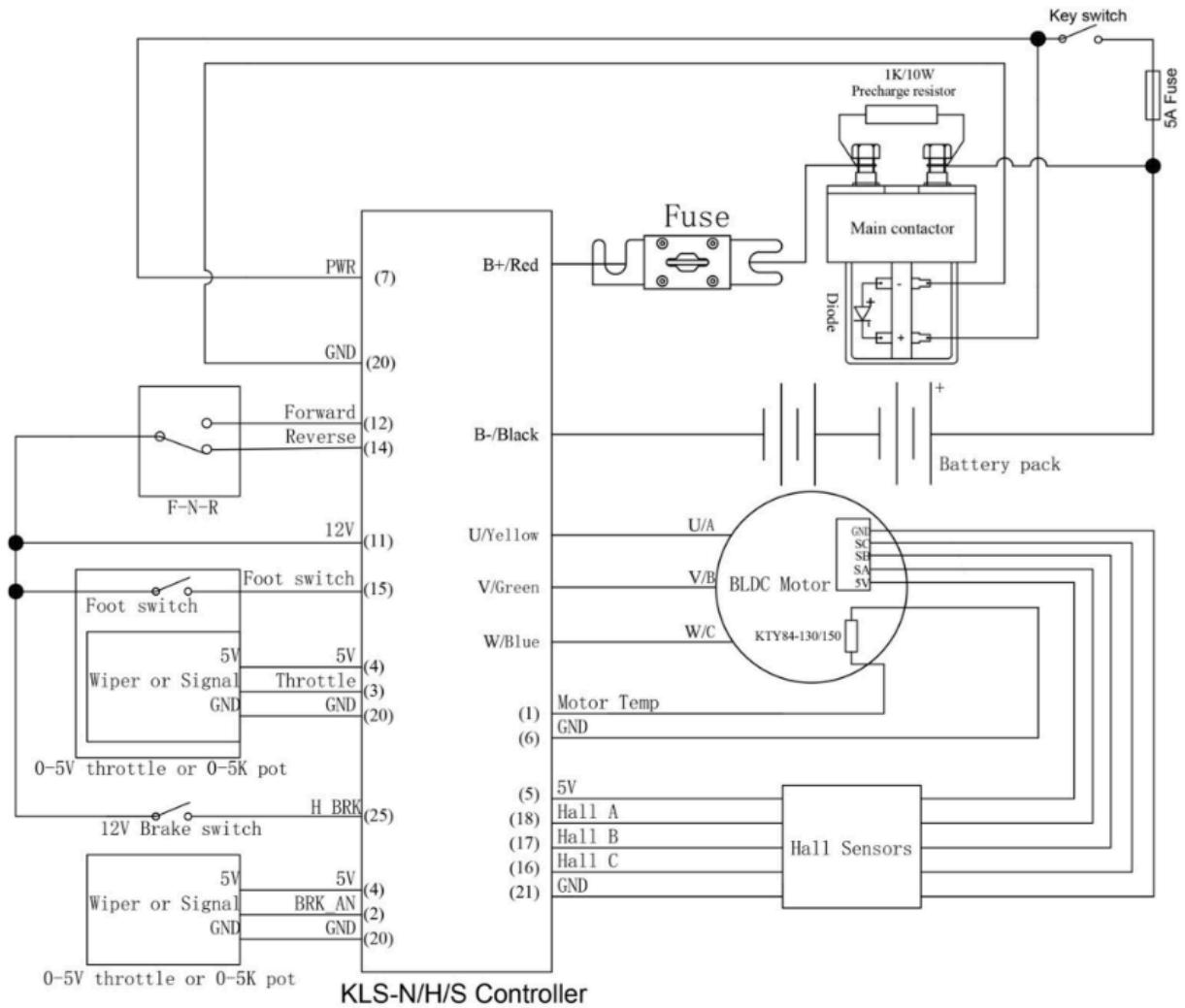

Pinout:

A

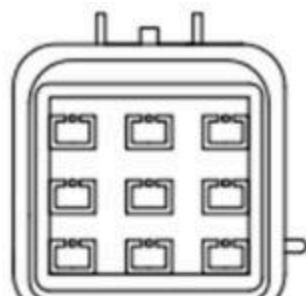

DJ7091Y-2.3-11

See from output side

Orange REV-SW (14)	Black GND (6)	White FWD (12)
Red 12V (11)	Yellowish 12V Brake (25)	Blue ECO (22)
Greenish CAN_H (33)	Pink PWR (7)	Brownish CAN_L (34)

B




DJ7091Y-2.3-21

See from output side

Gray Foot_SW (15)	Green Throttle (3)	
Black GND (20)	D-Gray Meter (8)	
Purple 5V (4)	Brown Brake_AN (2)	Red 12V (11)

C

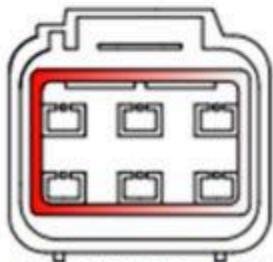

DJ7061Y-2.3-21

See from output side

Black GND (21)	Raddle Temp (1)	Purple 5V (5)
Yellow Hall A (18)	D-Green Hall B (17)	D-Blue Hall C (16)

## Conversion:

Connecting the **main cables** (battery power input and motor phase wires) is straightforward — the **terminal sizes and motor cable markings match well**.

To get the controller working, you need to connect at minimum:

- **A – Battery voltage** to **pin 7**
- **B – Throttle control**: connect to **pins 4 (signal)**, **20 (GND)**, and **3 (+5V)**
- **C – Hall sensors from the motor**: connect to **pins 5 (power)**, **21 (GND)**, and **16, 17, 18 (signal lines)**

## Optional but recommended:

- **Brake lever signal** → connect to **pin 25**
- **Motor temperature sensor** → connect to **pin 1**

## Additional optional features:

- **Reverse mode switching** → pin **14**
- **ECO mode toggle** → pin **22**

---

Connecting the **throttle** is simple: just wire up +5V, Signal, GND

These must match the voltage and pin expectations of both the throttle and the controller.

	Torrot	Kellys
+5V	3	<b>4</b>
signal	4	<b>3</b>
GND	5	<b>20</b>

## Wiring Hall Sensors and Power Supply

Wiring the **motor hall sensors** is also straightforward — it involves 3 signal wires and power lines.

- On the **Torrot**, the **+5V supply** is on **pin 17** → connect this to **Kellys pin 5**
  - Ground is on **Torrot pin 31** → connect to **Kellys pin 21**
  - The **signal wires** (Torrot pins 18, 19, 20) should be connected **according to their wire colors** to **Kellys pins 16, 17, 18**
- 

## Power Supply Considerations

Power for the controller comes from the **battery**, connected to **Kellys pin 7**. However, **do not use Torrot pin 34** for this. That pin is live **as soon as the battery is connected**, meaning the scooter would consume standby power even when parked — possibly not much, but it's a concern. Instead, I chose a method that follows the **Kellys wiring scheme** - The controller only receives power **after the key switch is turned on**.

**Pin 35** is also **not usable**, as it seems it originally powered the lower DC-DC converter. But after the key is turned, **this pin does not have voltage** — so it can't be used to power the controller either.

---

## The Problem: Original Torrot Switching Logic

The Torrot's original power switching setup was **partially handled by the controller**. It controlled power to the **secondary DC-DC converter**. It also controlled the **contactors** that connect the main battery. This logic also seems to involve the **display**, since the pink-white wire in the ignition harness goes to the display.



---

## The Solution: Simplified Ignition Switching

- Replace the **pink-white wire** going to the original display with a wire that sends **voltage from the key switch** to:
  - (a) The Kellys controller
  - (b) The **secondary DC-DC converter**
- Then, wire the **contactors** to be switched by **12V output from the secondary DC-DC**

This way, turning the key:

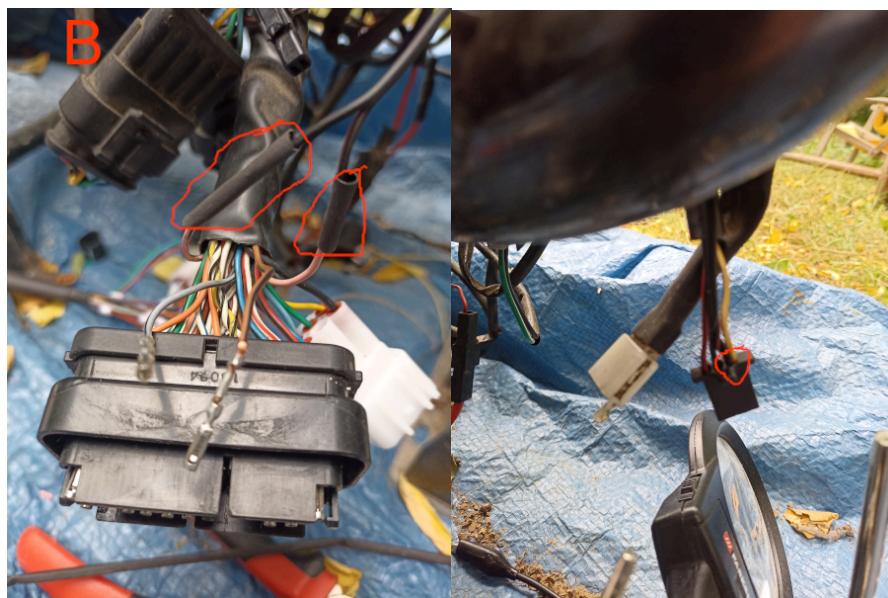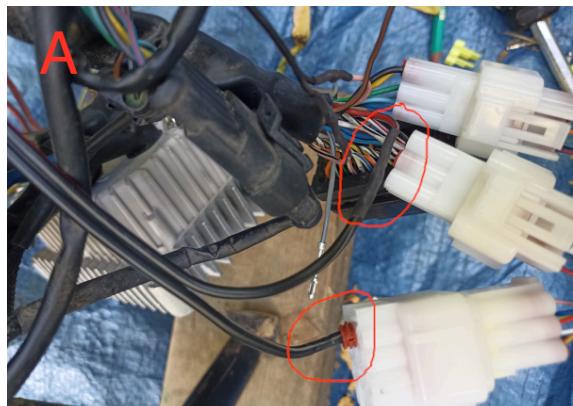- Powers the controller
- Powers the DC-DC converter
- And through it, switches on the contactors — safely connecting the battery



**A) Connect power from the ignition switch (key switch) to the Kellys controller**

→ and also use this to **power the secondary DC-DC converter** (this replaces the original function of pin 35).

**B) Take the 12V output from the secondary DC-DC converter** (available on the cable near its connector)

→ and route it to the **relay controlling the contactors** (which originally used pins 12 and 13 on the Torrot controller).

## Blinkers

The **turn signal switch** on the handlebars sends 12V to a signal wire (orange-black) that goes to the “9-pin” connector — specifically to the **gray and blue wires**, which originally went to **pins 11 and 11** of the controller.

We bring **12V from the Kellys controller (e.g., pin 11 or 11)** to the **signal pin**, and then use a **voltage divider** to step it down from **12V → 5V**, which feeds into an **Arduino input**.

The **blinkers (bulbs)** are grounded through the **original controller's pin 26**. This ground should now be connected to **Kellys pin 6 or 20**.


Blinkers are switched via the **Arduino output**, which drives **MOSFETs or relays** to supply **12V from the DC-DC converter** to the blinkers.

The control signals go through the **original wires that led to pins 23 and 24**. See photo.

---

I found it best to **cut the signal wire** from the turn signal switch near the “9-pin” connector on the handlebars, so that I could access **both sides of the wire**.

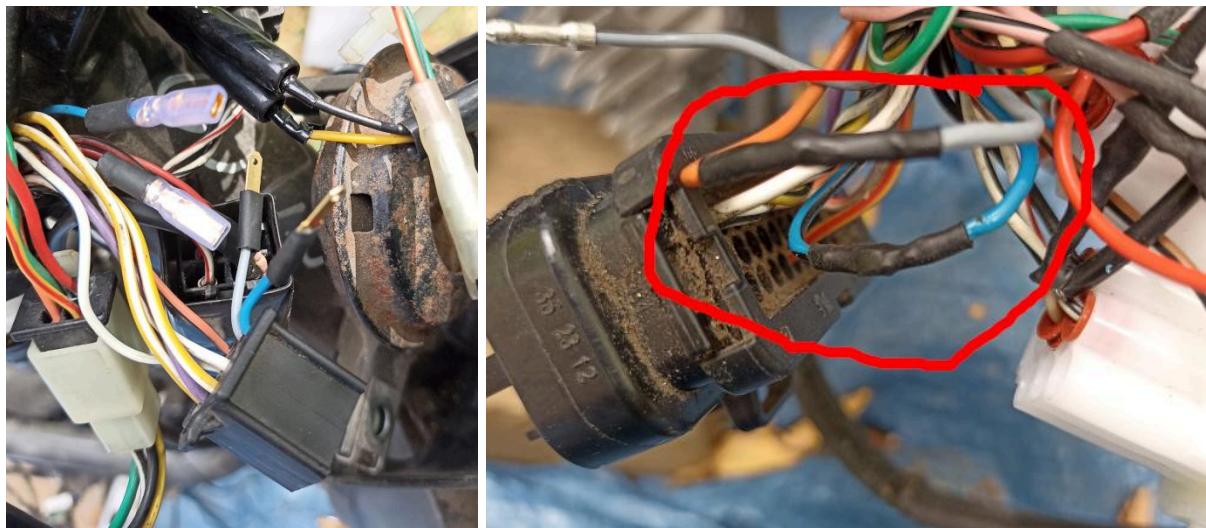- The **signal from the switch** goes to an **Arduino input**.
- The **Arduino output** then drives a **relay**, which sends **12V** to the original blinker signal wires.
- These wires lead down to the controller area, where I connected them to the **original signal wires** (10 and 11), which now drive the **relay/MOSFET switching lines** (23 and 24). See photo.



## Brake Switch (Lever Brakes)

The **brake switch** on the handlebars is **normally open (OFF)** by default.

When pressed, it sends a **12V signal** (from the same power branch used for the blinkers) to **pin 7**.

This **signal should be connected to Kellys controller pin 25**.

Additionally, the signal should be **split** so it can also be used to **switch the brake lights** (see next section).

---


## Rear Lights, Brake Lights, and Blinkers

- **Blinkers** do not require separate wiring — the **rear blinkers share the same circuit as the front**.
- The **rear lights** share a **common ground** with the blinkers (see previous "Blinkers" section) — just wire them up and they work.
- The **brake lights** were originally switched by the Torrot controller.

To replace this functionality:

- Either control them via the **Arduino**
- Or (preferably) **split the signal from the brake switch** (brown wire, pin 7 at the connector), and use it to **control a MOSFET or relay**, which then switches **12V from the DC-DC converter** to the brake lights.


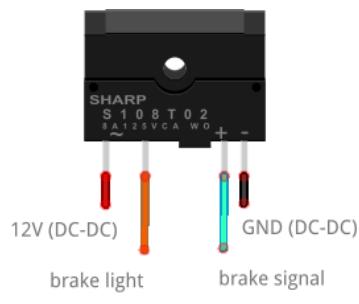
*A photo is missing, but a wiring diagram is included instead.*


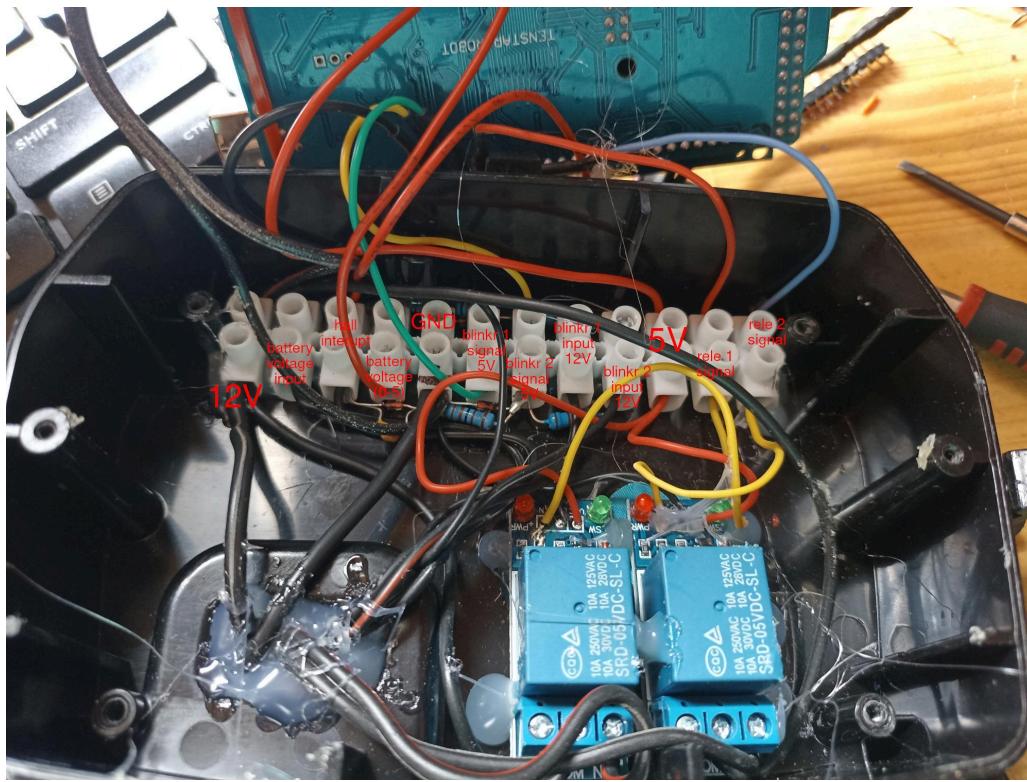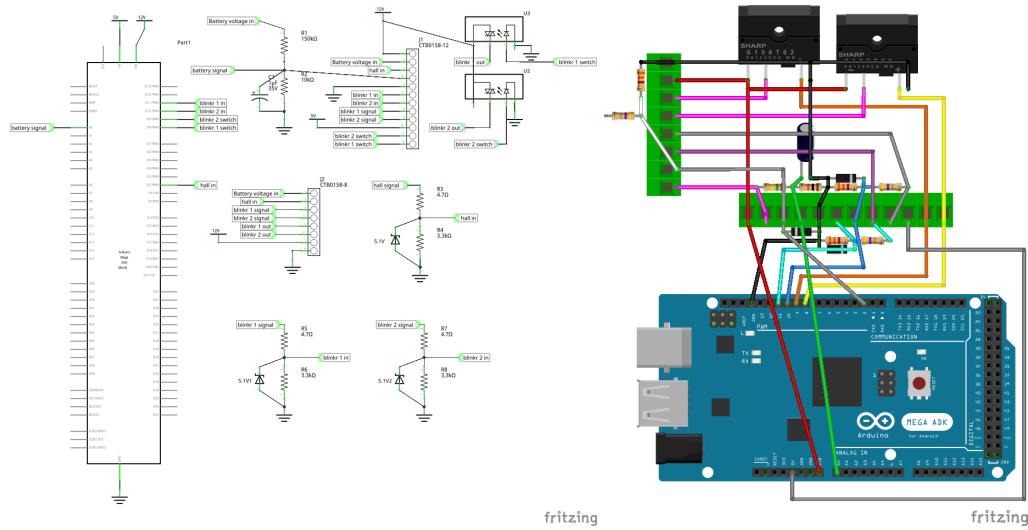
## Internal Display Wiring

The original display has been replaced with an **Arduino MEGA**, paired with a display shield - [3.5" 320x480 TFT display, ILI9486, Arduino Mega shield](#)

This custom setup serves as the new dashboard display in place of the factory CAN-bus display.



## Notes

It may be worth considering **not controlling the blinkers via the Arduino**, but instead using a **dedicated hardware blinker relay** (flasher unit), which would simplify the logic and reduce the load on the microcontroller.

---

## Kellys Controller Configuration

At minimum, the Kellys controller requires two configuration steps:

1. **Automatic identification of Hall sensors**  
→ Refer to the Kellys manual, pages 23–24.
2. **Disable regenerative braking**  
→ To avoid overvoltage issues, set the parameter **BRK\_SW Brk %** to **0** (this can be found on the second page of the configuration software).